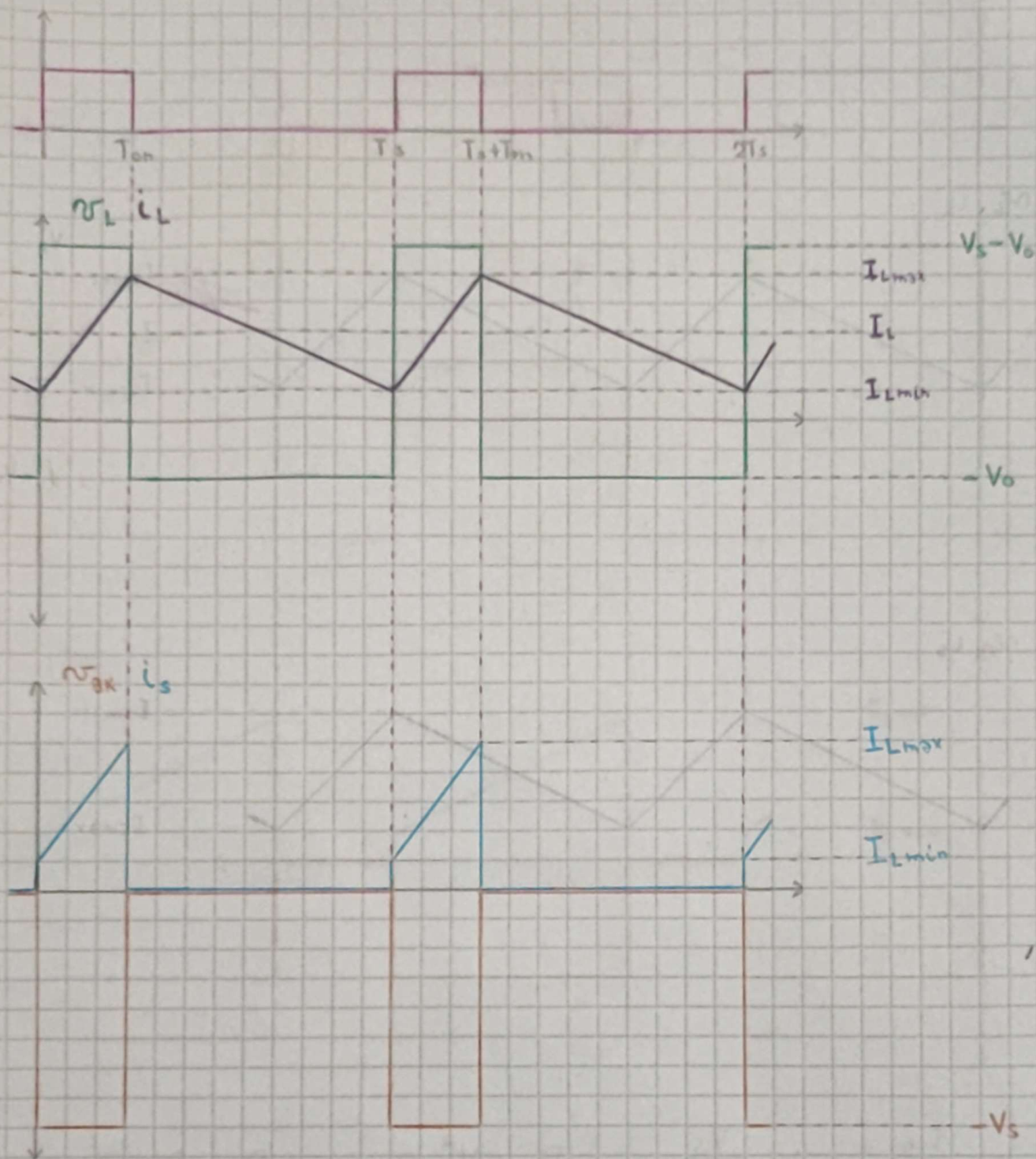


Convertidor-reductor



$$V_o = D \cdot V_s$$

$$V_o = 0,25 \cdot 20V$$

$$V_o = 5V$$

$$P_o = (V_o)^2 \cdot R$$

$$P_o = (5V)^2 \cdot 5\Omega$$

$$P_o = 125W$$

$$P_s = P_o$$


$$P_s = 125W$$

JOAQUÍN CHANQUÍA

02887/7

[Signature]

Convertidor - elevador

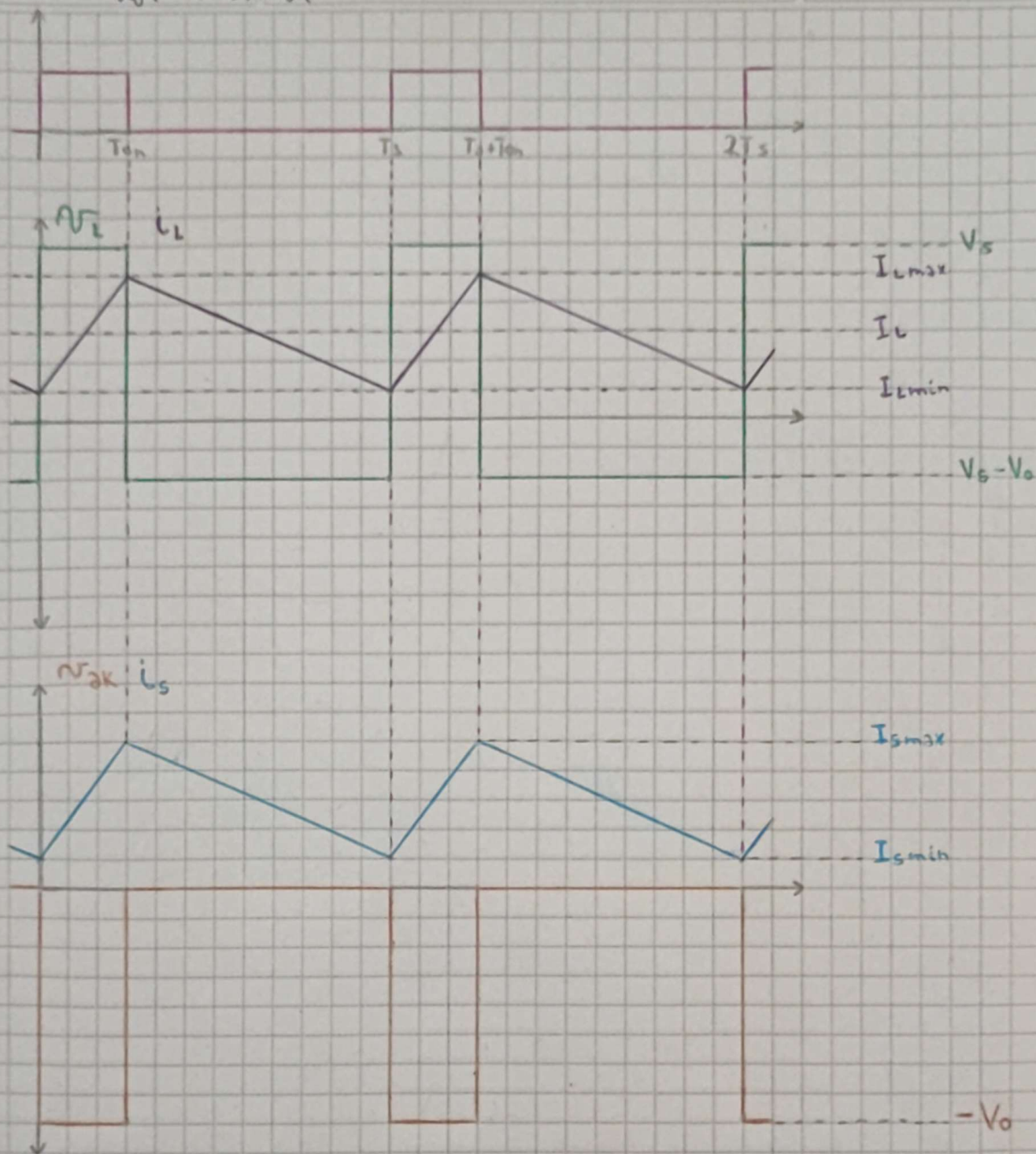

$$V_o = \frac{V_s}{(1-D)}$$

$$V_o = \frac{20V}{(1-0,25)}$$

$$V_o = 26,6V$$

$$P_o = (V_o)^2 R$$

$$P_o = (26,6V)^2 \cdot R$$

$$P_o = 3555,6W$$

$$P_s = P_o$$

$$P_s = 3555,6W$$

JOAQUÍN CHANQUÍA
02887/7

Joquin