
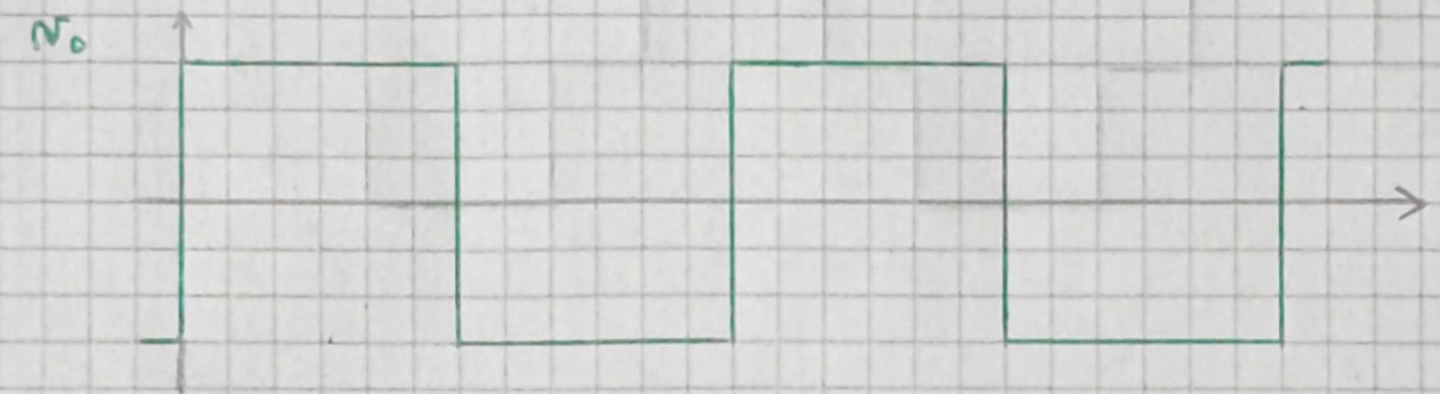


Onda Cuadrada

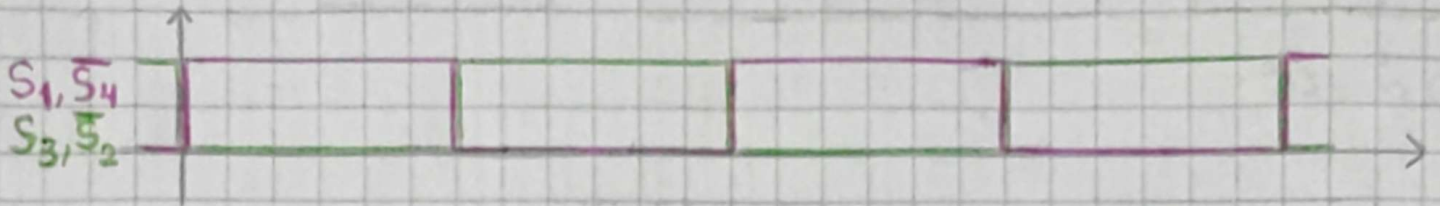




$$V_1 = \frac{4V_s}{\pi} = \frac{4 \cdot 300V}{\pi} = 381,971V$$

$$V_{1rms} = \frac{V_1}{\sqrt{2}} = \frac{381,97V}{\sqrt{2}} = 270,09V$$

PWM Monopulso

$$\alpha = 30^\circ$$

$$2\alpha = 60^\circ$$

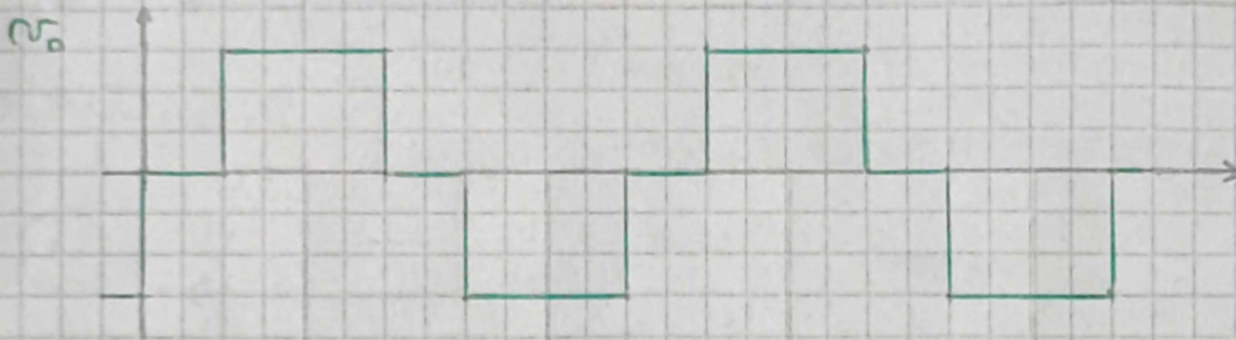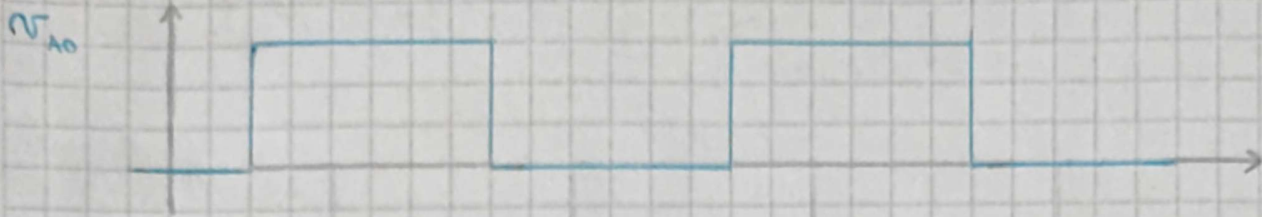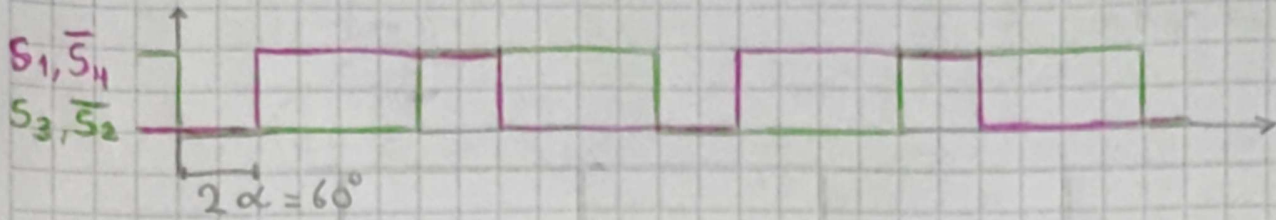

$$V_1 = \frac{4V_s}{\pi} \cos(\alpha) = \frac{4 \cdot 300V}{\pi} \cos(30^\circ) = 330,79V$$

$$V_{rms} = \frac{V_1}{\sqrt{2}} = \frac{330,797V}{\sqrt{2}} = 233,91V$$